

## Carry - look ahead adder

This method uses modified carry algorithm to reduce the time needed in ripple carry. This is because it divides carry out into two groups 'generate' and 'propagate' based on A & B. ~~total~~

When

$$A = B = 0$$

Carry out = 0  $\leftarrow$  No carry generate

$$A = B = 1$$

Carry out = 1  $\leftarrow$  carry generate

despite carry in value.

When

$$A = 0, B = 1$$

$$A = 1, B = 0$$

or  $\} \leftarrow$  carry propagate

carry out may, may not be 1 and depends on carry in.

$$P_i = A_i \wedge B_i$$

$$G_i = A_i \& B_i$$

$$S_i = P_i \oplus C_{in}$$

$$C_{out} = G_i + P_i C_{in}$$

Let  $C_1, C_2, C_3 \dots$  represent carry out.

$$C_1 = G_0 + P_0 C_{in}$$

$$C_2 = G_1 + P_1 C_1$$

$$C_3 = G_2 + P_2 C_2$$


and so on. Now,  $C_2$  can be written in terms of  $C_1$  and  $C_1$  in terms of  $C_{in}$ . So the ripple adder won't have to wait for carry to get calculated



## Johnson Counter

In Johnson counter, the complemented output of last flip flop is connected to first one.  
 Rest all flip-flops are directly connected

0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0
1	1	1	1	1	1	0	0	0	0
1	1	1	1	1	1	1	0	0	0
1	1	1	1	1	1	1	1	0	0
0	1	1	1	1	1	1	1	1	0
0	0	1	1	1	1	1	1	1	0
0	0	0	1	1	1	1	1	1	0
0	0	0	0	1	1	1	1	1	0
0	0	0	0	0	1	1	1	1	0
0	0	0	0	0	0	1	1	1	0
0	0	0	0	0	0	0	1	1	0
0	0	0	0	0	0	0	0	1	0

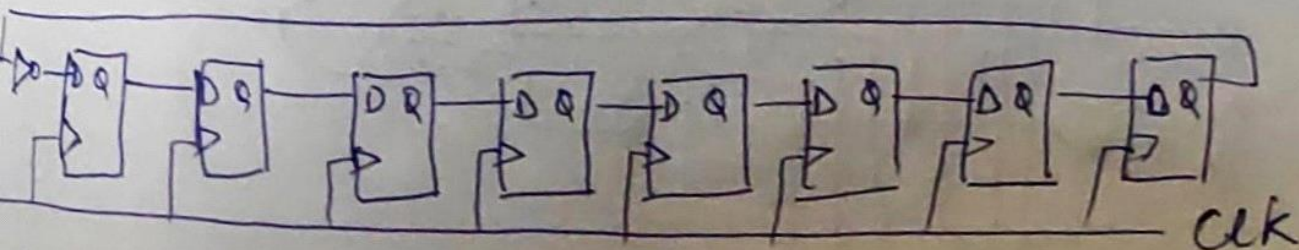

At each pos-edge of clock, the value from previous FF gets transferred to the next until it reaches the last FF. After that, the signal gets inverted and the process continues.



