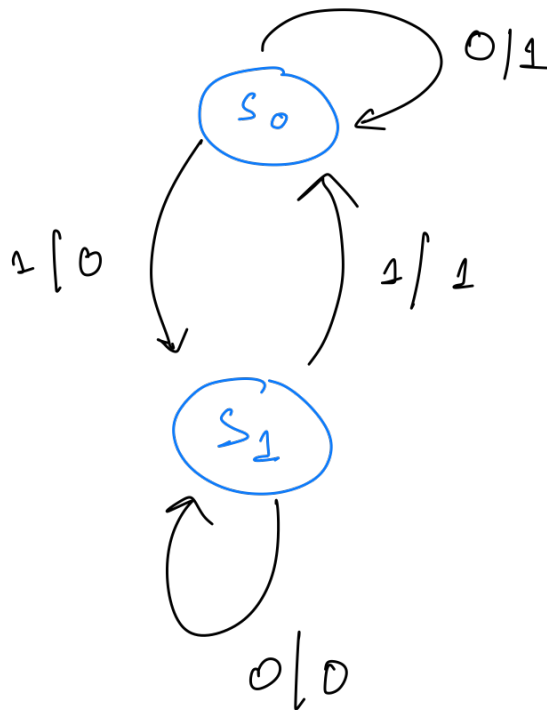


Q 2) odd parity generator

state diagram:



$S_0 \rightarrow$  initial state  
because no one  
has been encountered

$S_0$  : no. of 1s encountered  
after blank  
input are even

$S_1$  : no. of 1s encountered  
after blank  
input are odd

next odd parity generator  $\Rightarrow$  generates parity of last  
received bit (n-1)th output bit.

next signal sent after 4 time units.

State Table:

PS	Next state, output	
	In	
	0	1
0	(0, 1)	(1, 0)
1	(1, 0)	(0, 1)

Transition and Output table:

PS	Next state $T_n$		Output $T_n$	
	0	1	0	1
0	0	1	1	0
1	1	0	0	1

2 states, we can use a D-flip flop

Excitation Table:

PS $a$	Input $b$	NS $a'$	FF input $D$	O/p $o$
0	0	0	0	1
0	1	1	1	0
1	0	1	1	0
1	1	0	0	1

## K Maps

D

a \ i	0	1
	0	1
0	0	1
1	1	0

$$D = \bar{a} \cdot \bar{i} + a \cdot \bar{i}$$

$$D = a \oplus i$$

0

a \ i	0	1
	0	1
0	1	0
1	0	1

$$0 = \bar{a} \cdot i + a \cdot i$$

$$0 = y \cdot i$$

## Circuit diagram

